

Assignment 2

Class- SE IV

Roll NO-21430

Batch- F4

DOS.

Title- Design and implement code convertor
Binary to gray and BCD to Excess-3.


Objective:-

1. Design and implement 4 bit binary to gray code converter using minimum number of logic gates and vice-versa.
2. Design and implement excess-3 to BCD code converter using minimum number of logic gates and vice-versa.

Apparatus:- Digital board, GP-6 patch cords,
IC-74LS85, IC 74LS32, IC-74LS08 / IC-74LS04
and required logic gates if any

Theory- Code converter is combinational logic circuits which can be used to convert one number system to another. Binary code is a weighted code having base 2. Gray code is code in which one in which bit change is obtained. Gray code BCD is 4 bit code but it is valid from 0 to 9. Excess-3 are valid from 3 to 15. Excess 3 is non-weighted code. It is sequential or self-complementary code.

Pin Diagram:-

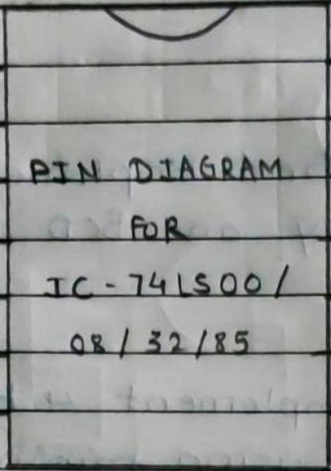1A		Vcc
1B		4B
1Y		4A
2A		4Y
2B		3B
2Y		3A
GND		3Y

Procedure:-

1. Make the connections as per the logic circuit of 4 bit binary to 4 bit gray code converter and vice-versa and verify the truth table.
2. Make the connections as per the logic circuit of 4 bit BCD to 4 bit Excess-3 code converter and vice-versa and verify the truth Table.

* Design of 4 bit binary to gray code:-

* Truth Table:-

Bin. Eq	Binary Code Input				Gray code output			
	B ₃	B ₂	B ₁	B ₀	G ₃	G ₂	G ₁	G ₀
1	0	0	0	0	0	0	0	0
2	0	0	0	1	0	0	0	1
3	0	0	1	0	0	0	1	1
4	0	0	1	1	0	0	1	0
5	0	1	0	0	0	1	1	0
6	0	1	0	1	0	1	1	1
7	0	1	1	0	0	1	0	1
8	0	1	1	1	0	1	0	0
9	1	0	0	0	1	1	0	0
10	1	0	0	1	1	1	0	1
11	1	0	1	0	1	1	1	1
12	1	0	1	1	1	1	1	0
13	1	1	0	0	1	0	1	0
14	1	1	0	1	1	0	1	1
15	1	1	1	0	1	0	0	1
16	1	1	1	1	1	0	0	0

* K-Map Simplification for G₃, G₂, G₁, G₀.

B ₃ B ₂	B ₁ B ₀ 00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

$$G_3 = B_3$$

B ₃ B ₂	B ₁ B ₀ 00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1

$$G_1 = B_2 \oplus B_1$$

B ₃ B ₂	B ₁ B ₀			
	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1


$$G_2 = B_3 \oplus B_2$$

B ₃ B ₂	B ₁ B ₀			
	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$G_0 = B_1 \oplus B_2$$

* Logic Diagram:-

B₃ B₂ B₁ B₀

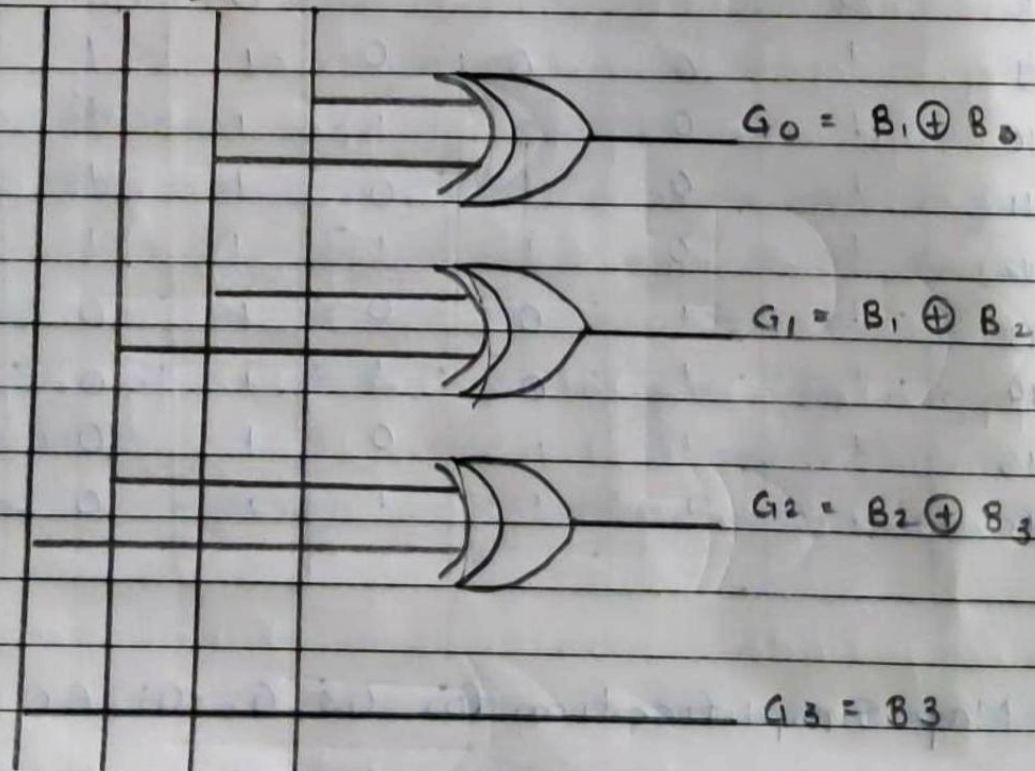

* Design of BCD code to Excess-3 Converter

No	Input BCD code				output Excess-3 code			
	B3	B2	B1	B0	E3	E2	E1	E0
1	0	0	0	0	0	0	1	1
2	0	0	0	1	0	1	0	0
3	0	0	1	0	0	1	0	1
4	0	0	1	1	0	1	1	0
5	0	1	0	0	0	1	1	1
6	0	1	0	1	1	0	0	0
7	0	1	1	0	1	0	0	1
8	0	1	1	1	1	0	1	0
9	1	0	0	0	1	0	1	1
10	1	0	0	1	1	1	0	0
11	1	0	1	0	1	1	0	1
12	1	0	1	1	1	1	1	0
13	1	1	0	0	1	1	1	1
14	1	1	0	1	x	x	x	x
15	1	1	1	0	x	x	x	x
16	1	1	1	1	x	x	x	x

* K-Map.

B3B2	B1B0			
	00	01	11	10
00				
01		1	1	1
11	1	x	x	x
10	1	1	1	1

$$E_3 = B_2(B_0 + B_1) + B_3$$

B3B2	B1B0			
	00	01	11	10
00		1	1	1
01	1			
11	1	x	x	x
10		1	1	1

$$E_2 = \bar{B}_2(B_0 + B_1) + B_0\bar{B}_1\bar{B}_2$$

B ₃ B ₂		B ₁ B ₀			
		00	01	11	10
00		1		1	
01		1		1	
11		1	x	x	x
10		1		1	


$$E_1 = B_2 (B_0 + B_1) + B_3$$

B ₃ B ₂		B ₁ B ₀			
		00	01	11	10
00		1			1
01		1			1
11		1	x	x	x
10		1			1

$$E_0 = \bar{B}_0$$

* Logic Diagram -

B₃ B₂ B₁ B₀

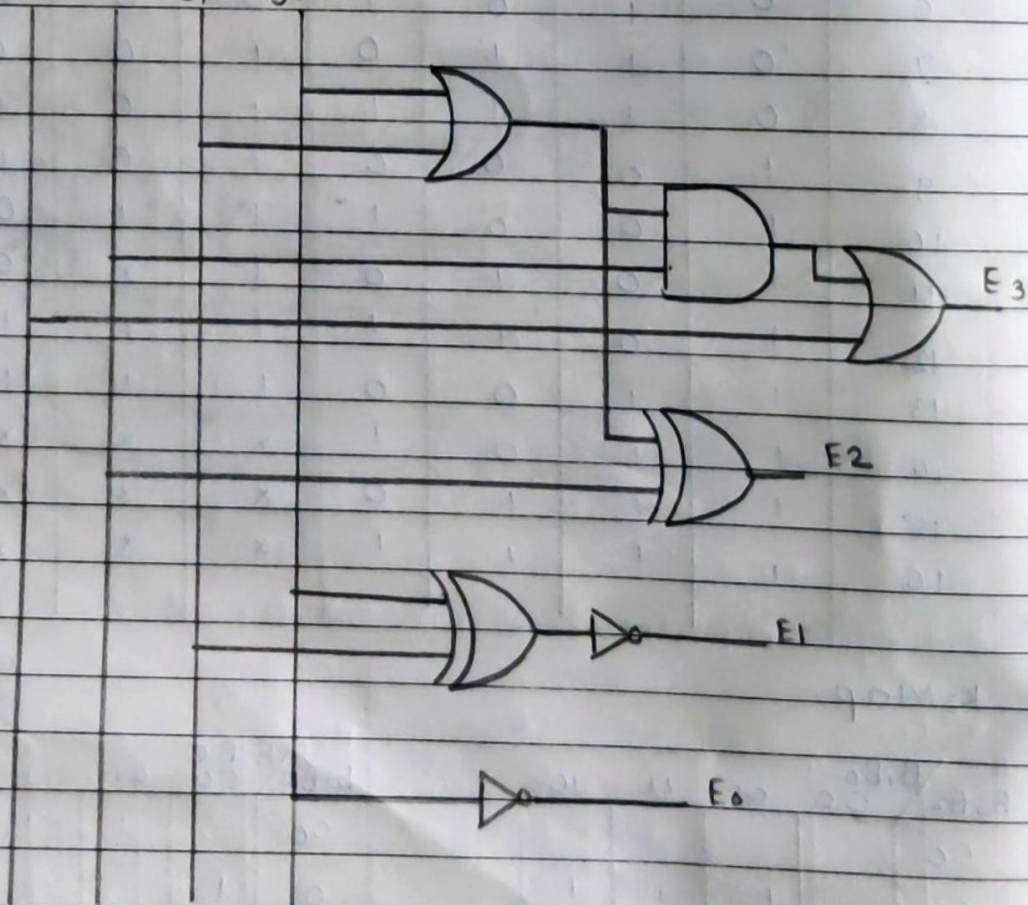

Logic gates / MSI device required for.

No.	Title.	Name of Ic	No. of gates	Ic required
1.	Binary to gray code	EX-OR	3	74LS86
2.	BCD to excess - 3	NOT	2	74LS04
		EX-OR	2	74LS86
		AND	1	74LS08
		OR	2	74LS32

Conclusion:-

Successfully implemented Binary to Gray code Converter and BCD to Excess-3 code Converter on an online digital trainer kit.



